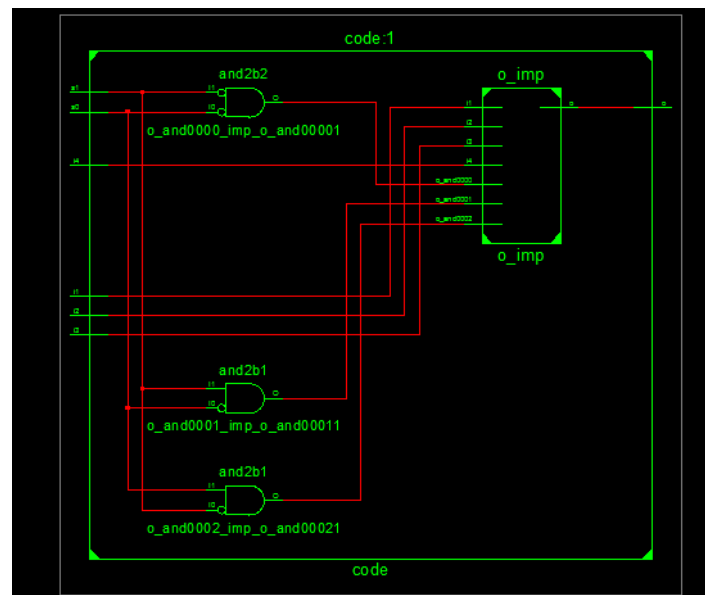



VLSI LAB REPORT  
K. Avinash, COE12B009  
XILINX

## Experiment 1: 4x1 MUX

### RTL Schematic



### Technology Schematic

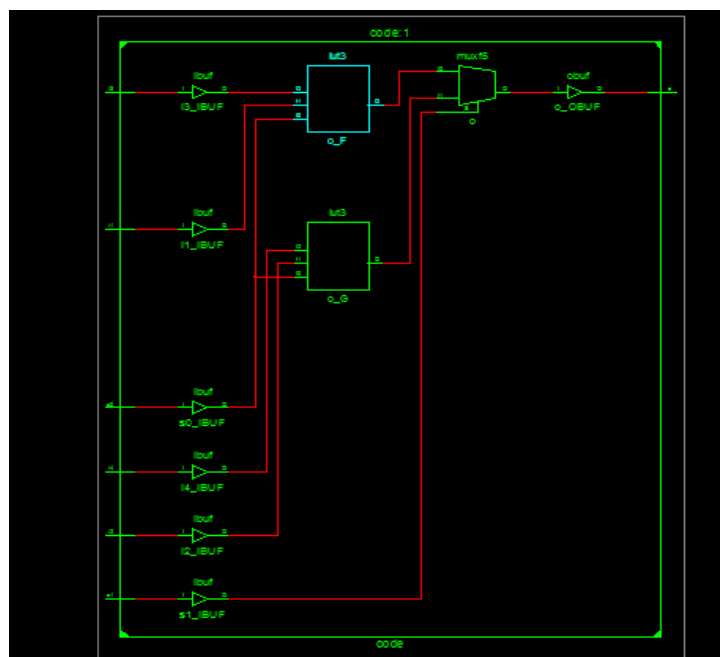


### Design statistics:


Number of Slices	:	1
Number of 4 input LUTs	:	2
Number of IOs	:	7
Number of bonded IOBs	:	7
Delay	:	6.054ns (Levels of Logic = 4)

## Experiment 2: Priority Encoder

### RTL Schematic

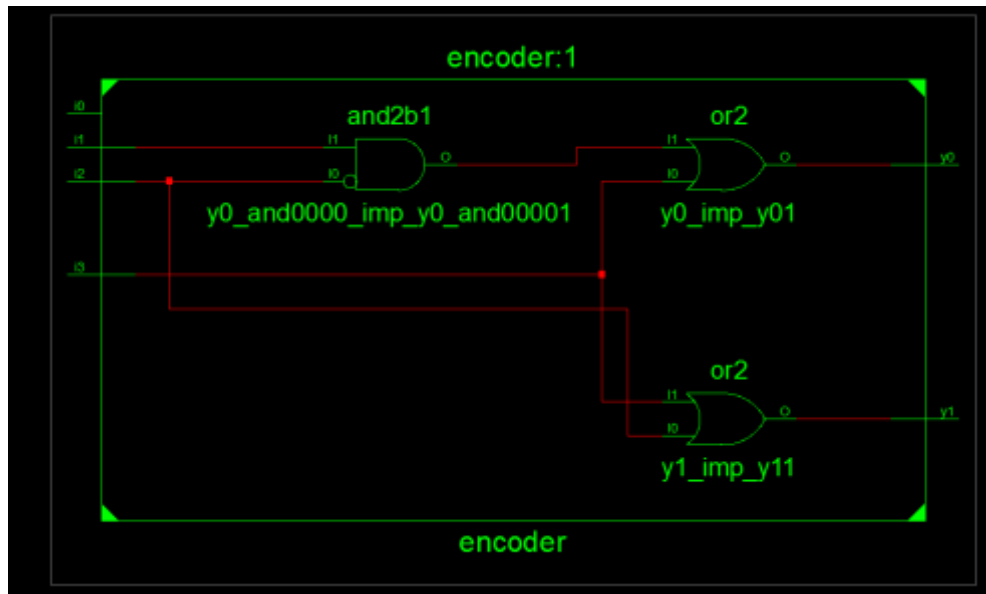

### Technology schematic

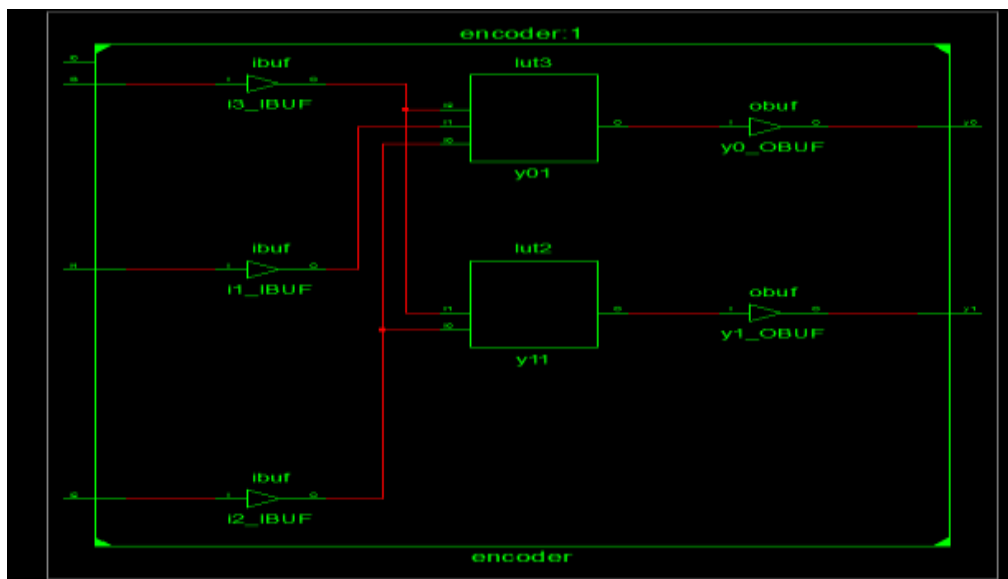


### Design Statistics:


Number of Slices	:	1
Number of 4 input LUTs	:	2
Number of IOs	:	6
Number of bonded IOBs	:	5
Delay	:	5.776ns (Levels of Logic = 3)

### Experiment-3: Decoder

#### RTL Schematic

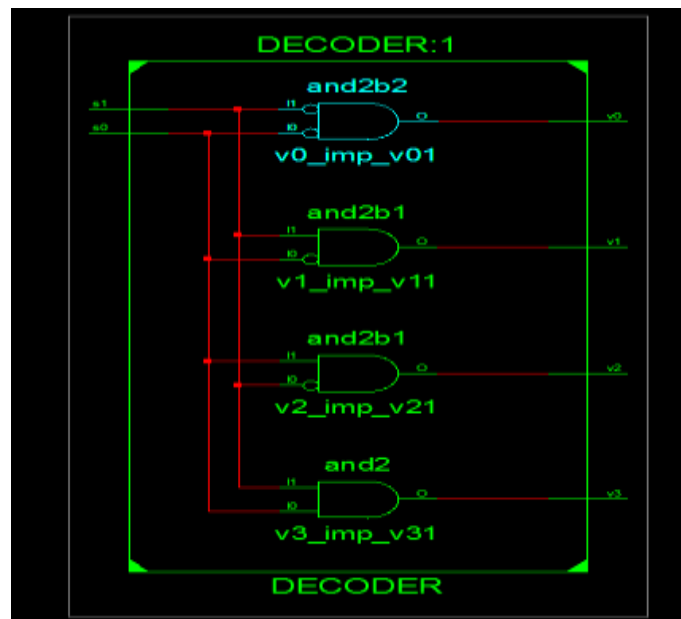

#### Technology Schematic

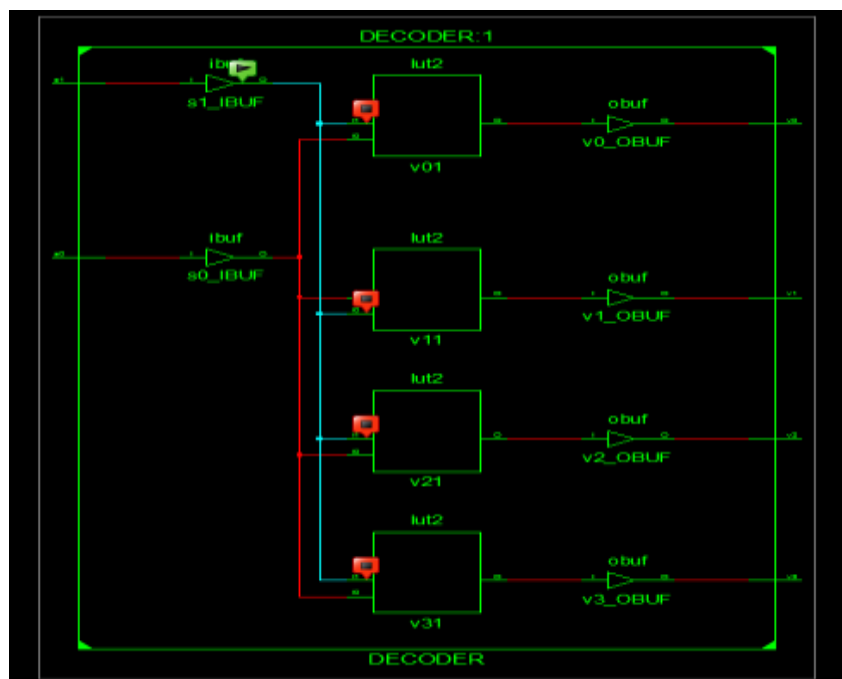


#### Design statistics:


Number of Slices	:	2
Number of 4 input LUTs	:	4
Number of IOs	:	6
Number of bonded IOBs	:	6
Delay	:	5.895ns (Levels of Logic = 3)

## Experiment-4: Full adder using half adders

### RTL Schematic

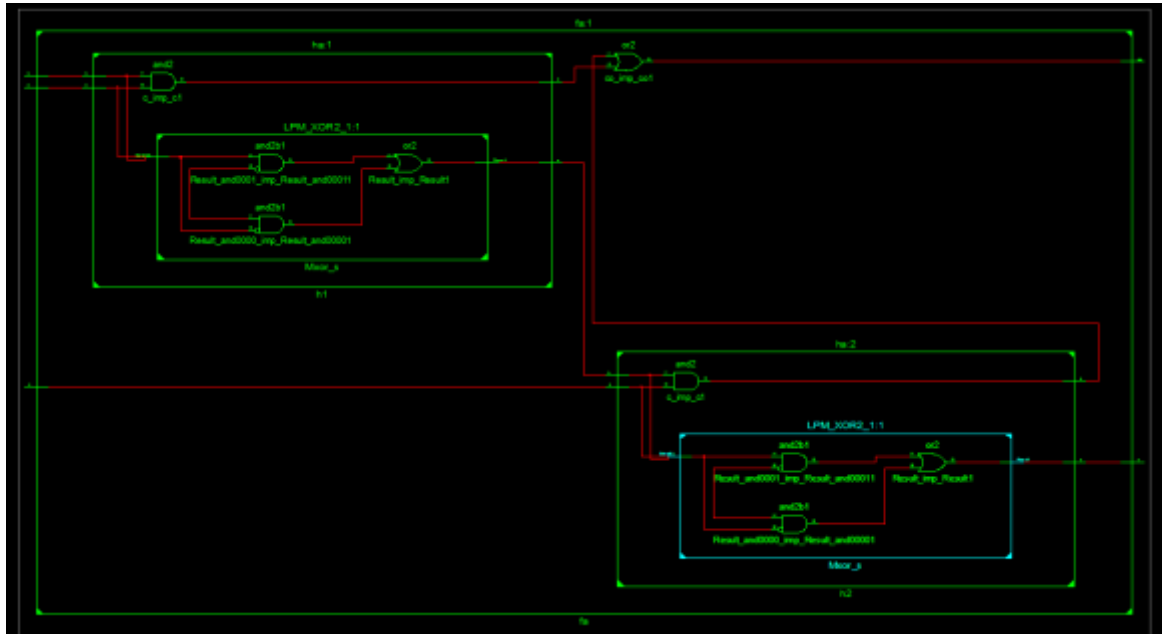

### Technology Schematic

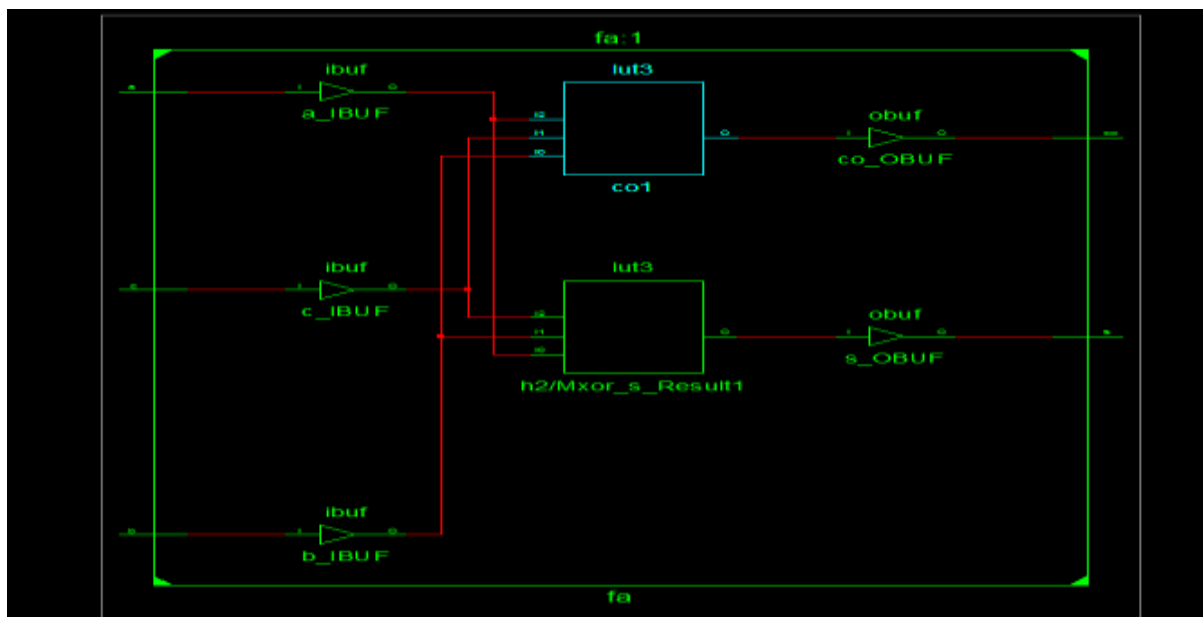


### Design statistics


Number of Slices	:	1
Number of 4 input LUTs	:	2
Number of IOs	:	5
Number of bonded IOBs	:	5
Delay	:	5.776ns (Levels of Logic = 3)

## Experiment 5: Binary to XS 3 Converter

### RTL Schematic

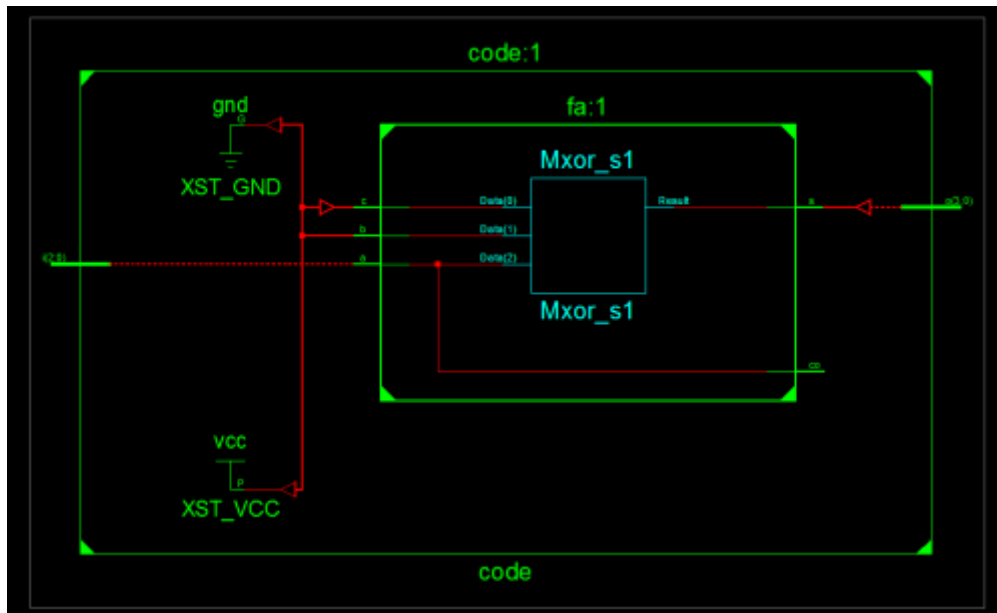

### Technology Schematic

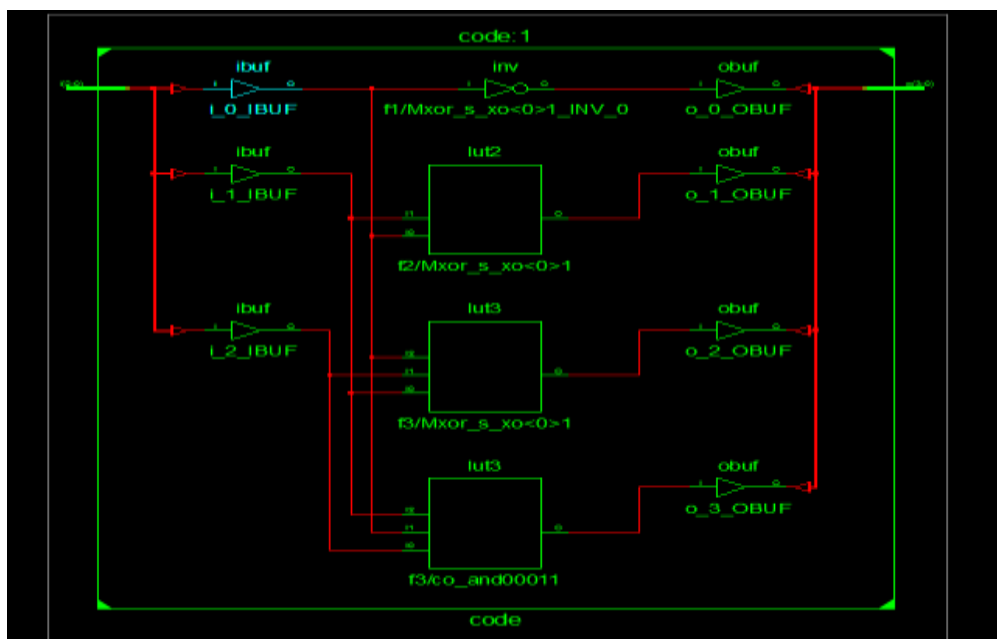


### Design statistics


Number of Slices	:	2
Number of 4 input LUTs	:	4
Number of IOs	:	7
Number of bonded IOBs	:	7
Delay	:	5.895ns (Levels of Logic = 3)

## Experiment 6: 2 bit multiplier

### RTL Schematic

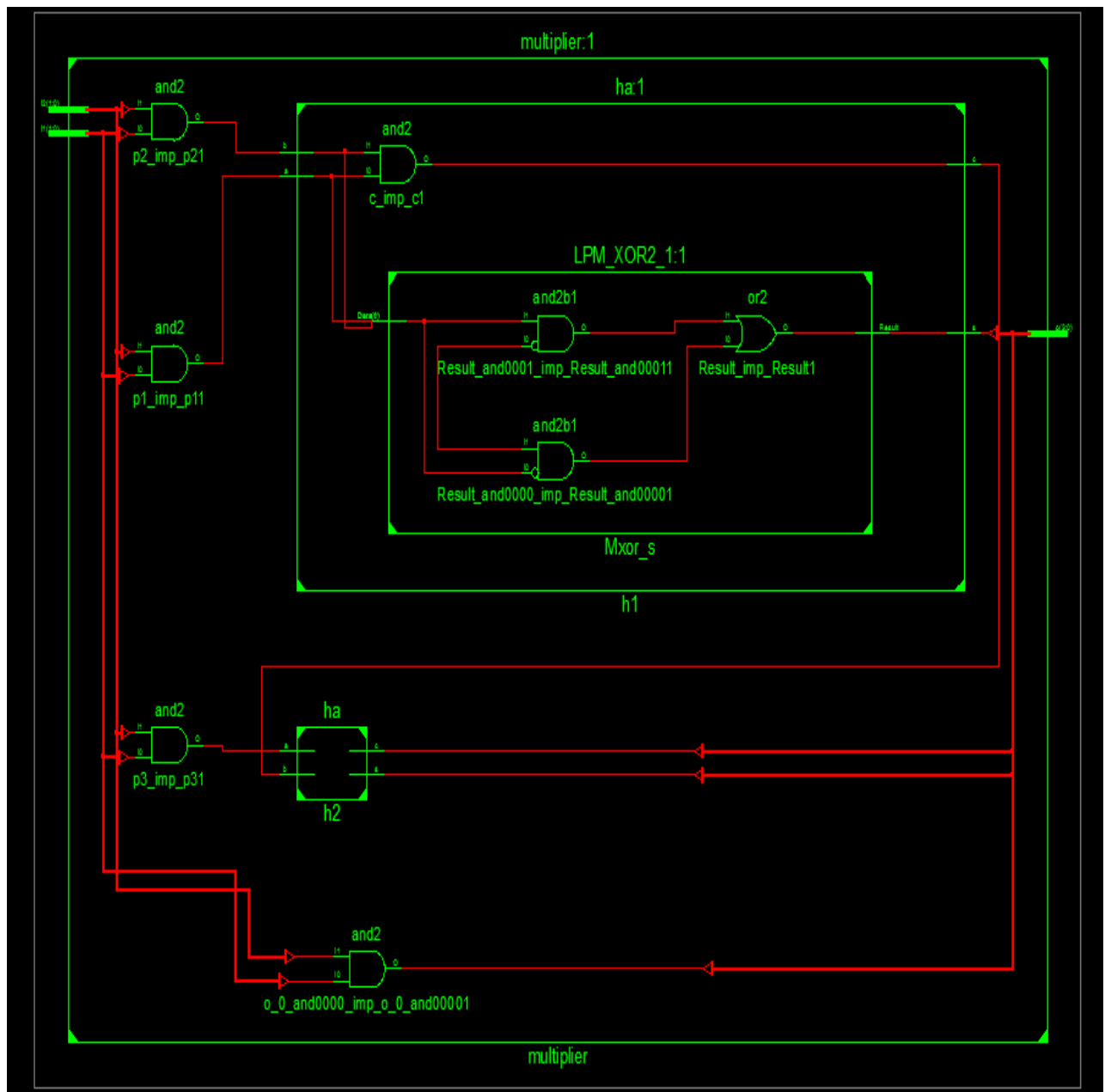

## Technology Schematic

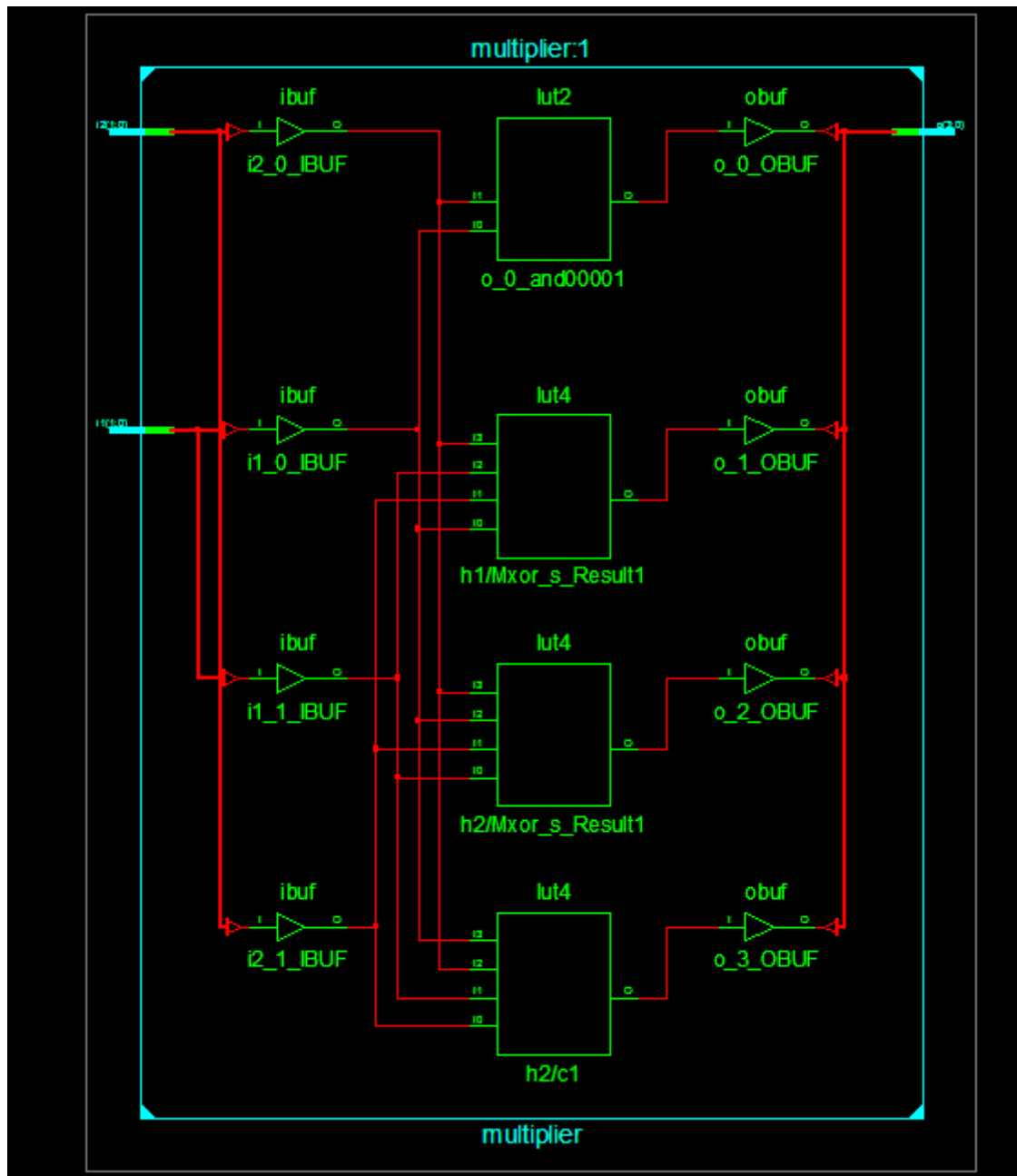


### Design statistics:

Number of Slices	:	2
Number of 4 input LUTs	:	4
Number of IOs	:	8
Number of bonded IOBs	:	8
Delay	:	5.895ns (Levels of Logic = 3)




## Experiment 7: Latch

### RTL Schematic

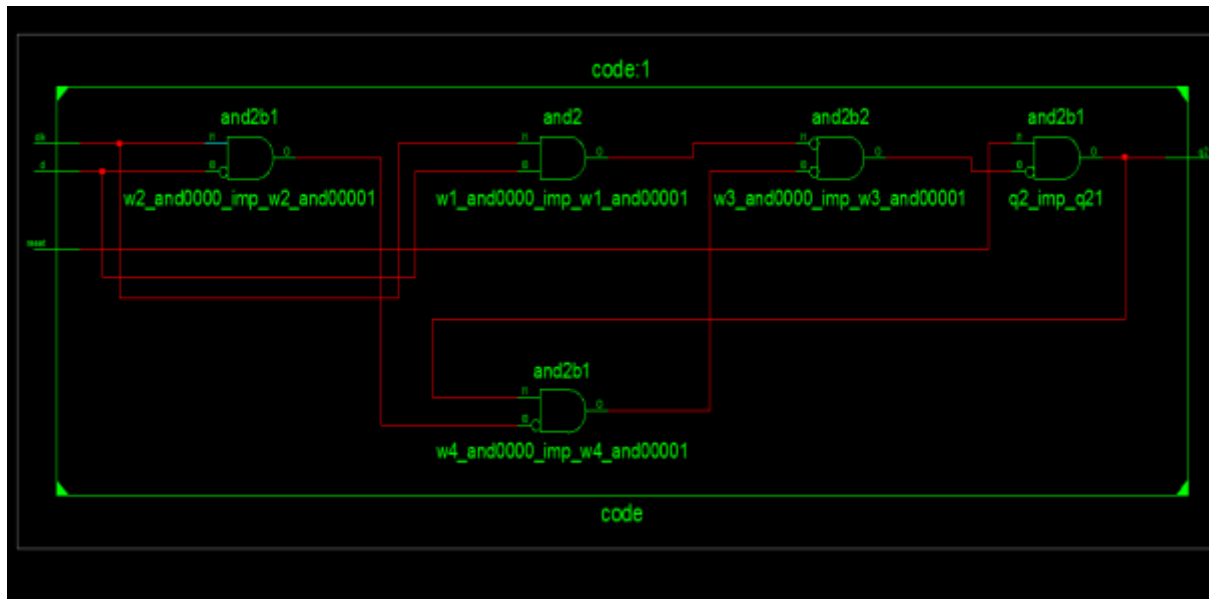

### Technology Schematic

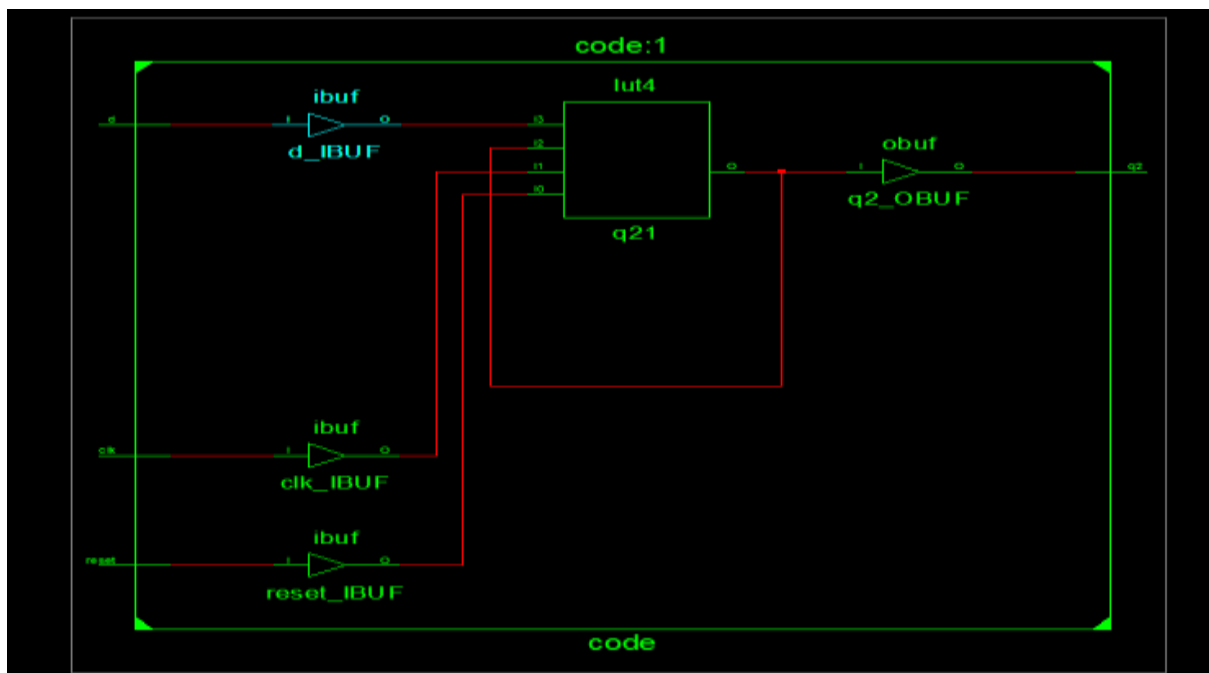


### Design statistics


Number of Slices	:	1
Number of 4 input LUTs	:	1
Number of IOs	:	4
Number of bonded IOBs	:	4
Delay	:	5.776ns (Levels of Logic = 3)

## Experiment-8: D Flip flop

### RTL Schematic

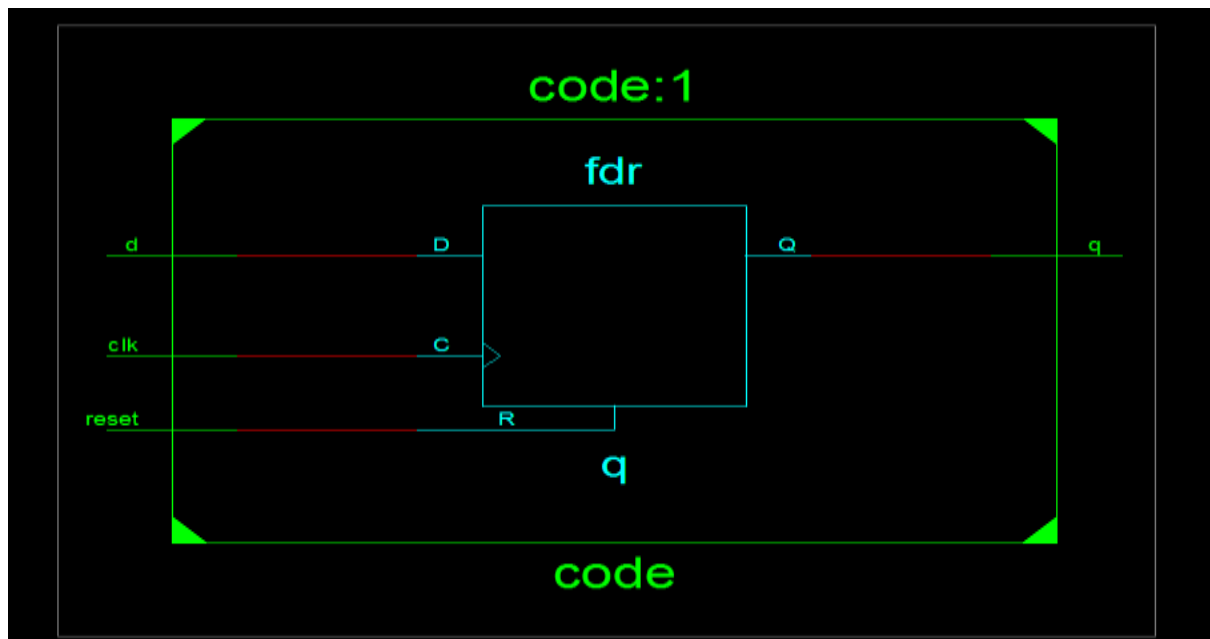

### Technology Schematic

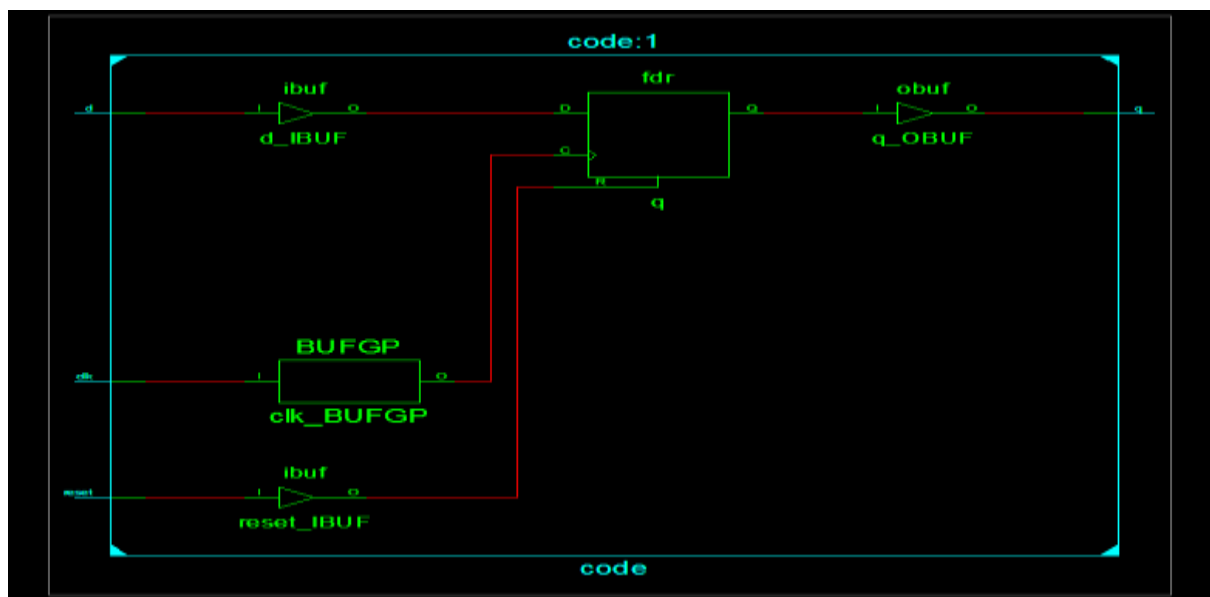


### Design Statistics


Number of Slices	:	0
Macros	:	1 Registers, 1 Flip-flops
Number of IOs	:	4
Number of bonded IOBs	:	4
Delay	:	Before clock: 2.258ns, after clock: 4.04ns

Experiment-9: Boundary scan register

RTL Schematic

 

## Technology Schematic

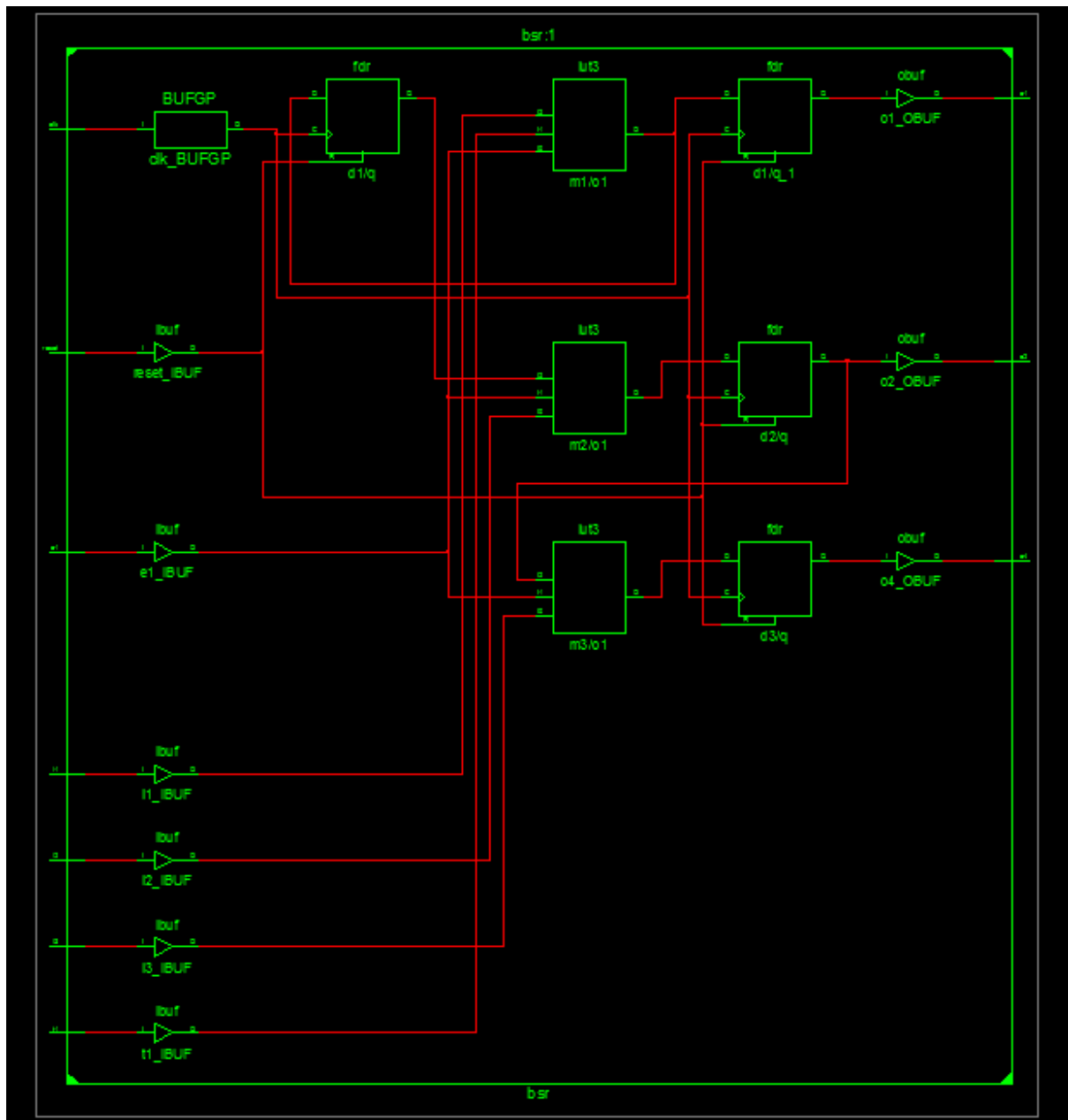


## Design statistics


Number of Slices	:	2
Number of 4 input LUTs	:	3
Number of IOs	:	10
Number of bonded IOBs	:	10
Macros	:	4 Register, 4 Flip-Flops
Delay	:	Before clock: 2.589ns, after clock: 4.063ns

## Experiment-10: Binary to XS 3 Parallelization

### RTL Schematic

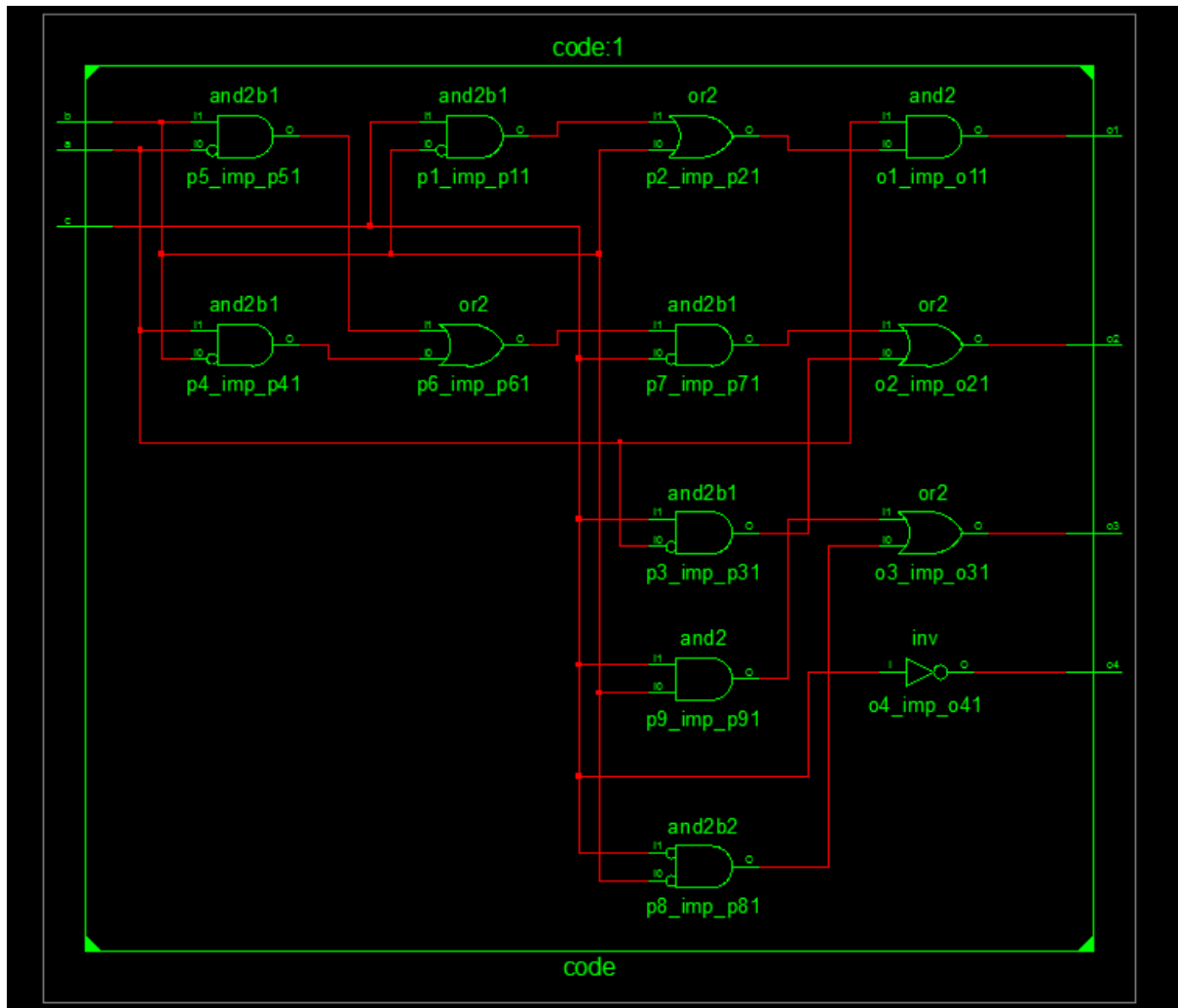

## Technology Schematic

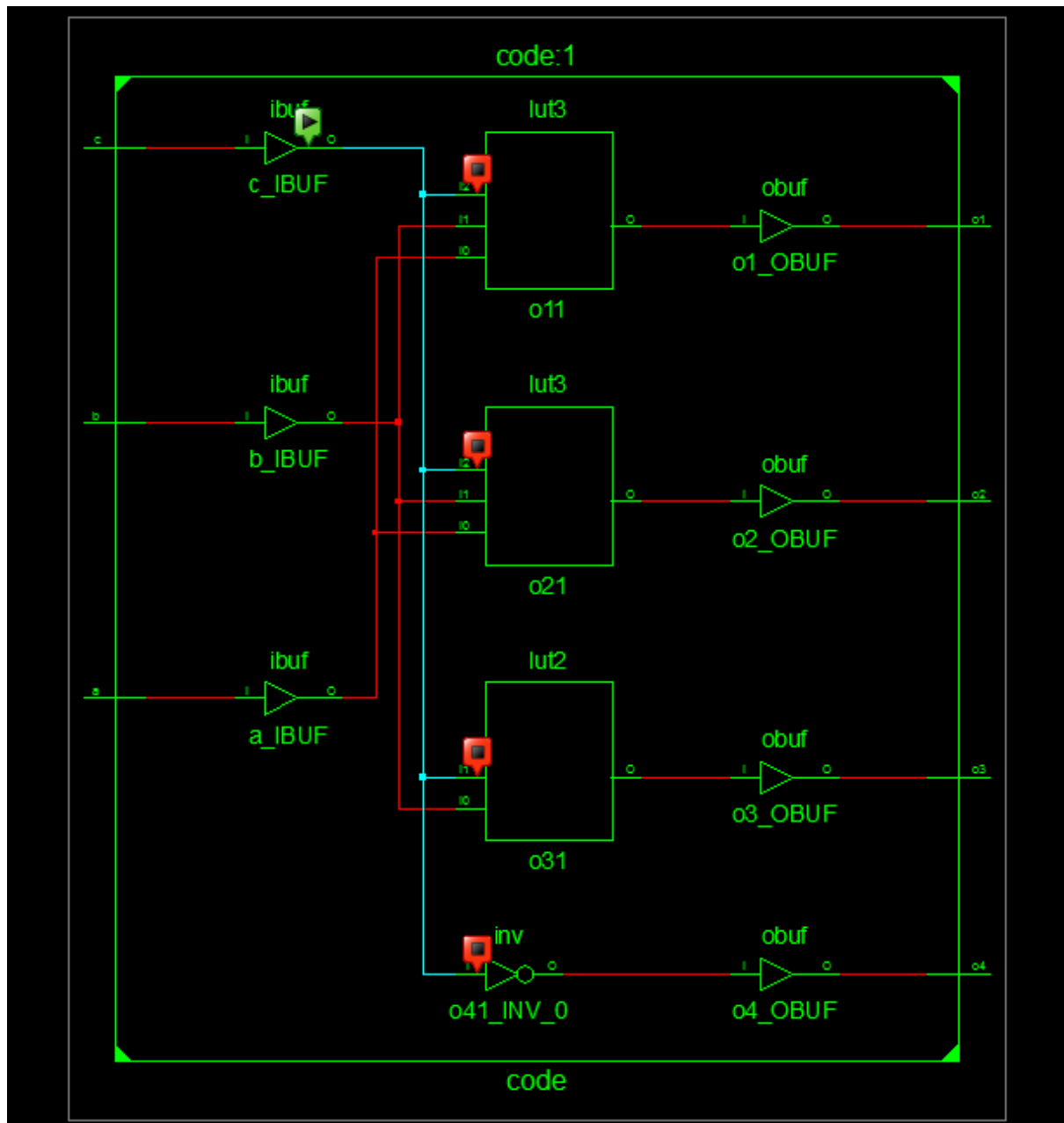


## Design Statistics


Number of Slices	:	1
Number of 4 input LUTs	:	2
Number of IOs	:	7
Number of bonded IOBs	:	7
Delay	:	6.054ns (Levels of Logic = 4)

Experiment-11: Moore finite state machine (Sequence 10100)

State Diagram

 


RTL Schematic

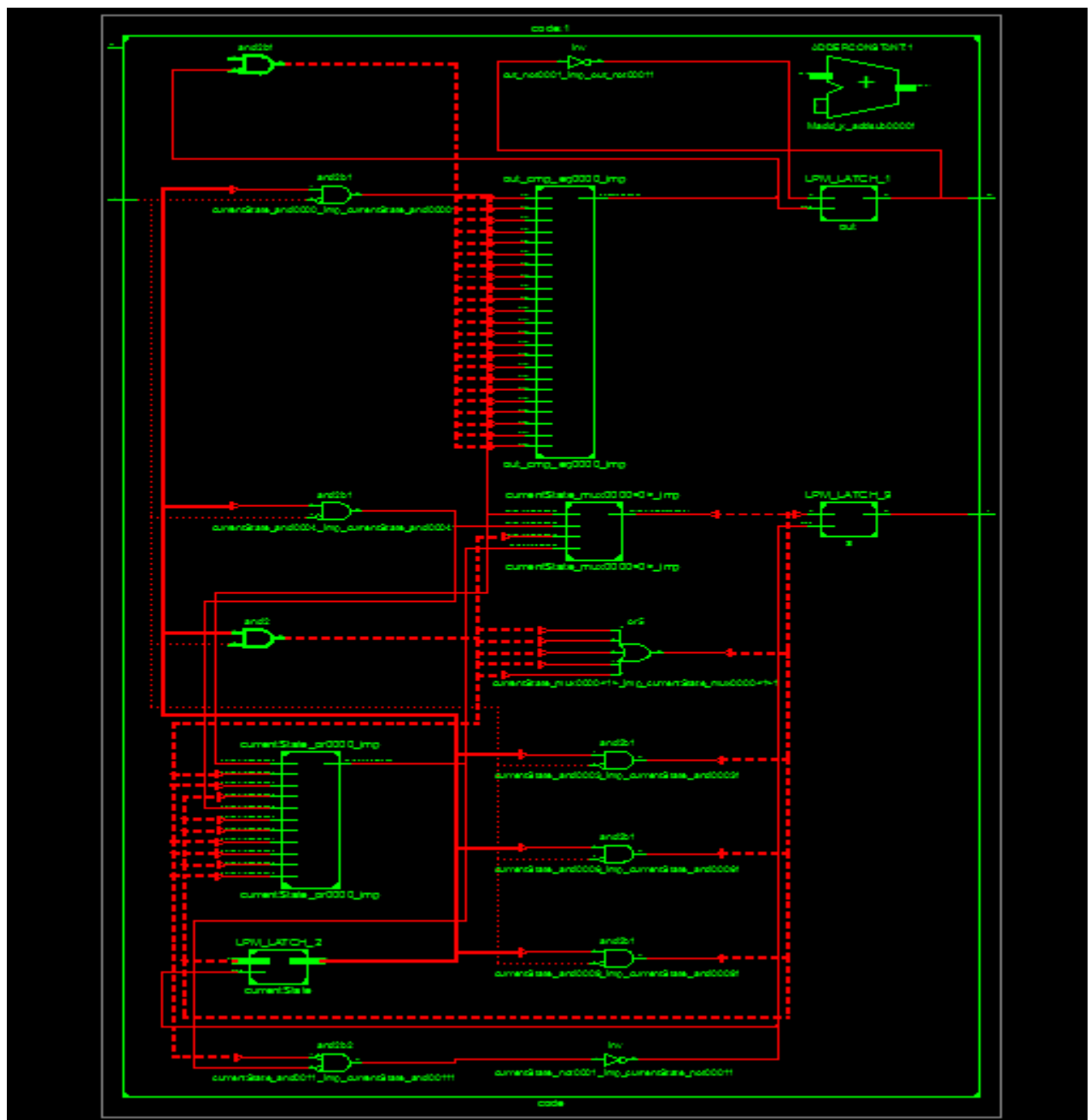



## Technology Schematic

 


## Design Statistics


Number of Slices	:	33
Number of 4 input LUTs	:	61
Number of IOs	:	4
Number of bonded IOBs	:	4
Delay	:	Before clock: 2.054ns, after clock: 4.208ns

## Experiment-12: Booth multiplier (4 Bit)

### RTL Schematic

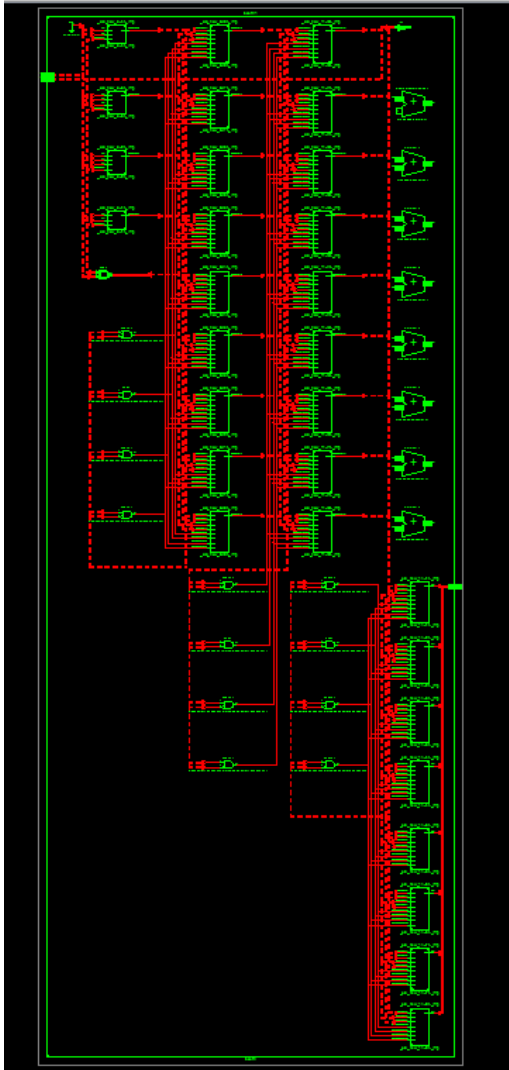

## Technology schematic

 


## Design Statistics


Number of Slices	:	21
Number of 4 input LUTs	:	37
Number of IOs	:	16
Number of bonded IOBs	:	16
Delay	:	14.205ns (Levels of Logic = 12)

## Experiment 13 D\_TO\_JK Flip-flop

### RTL Schematic

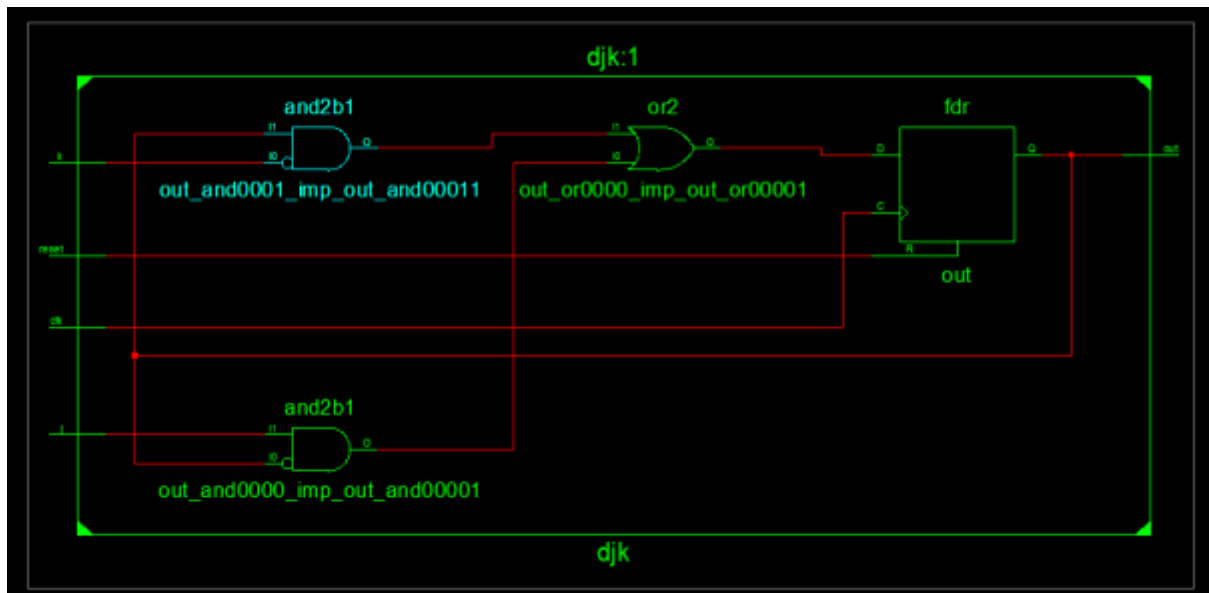


Technology Schematic

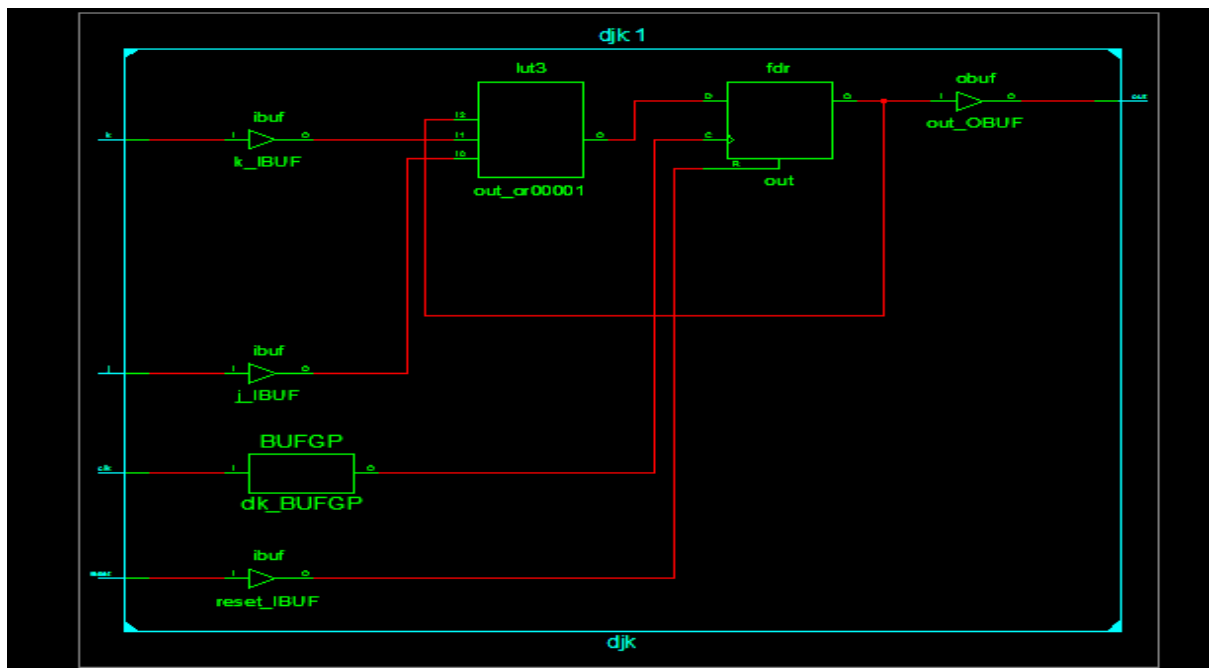

### Design statistics

Number of Slices	:	1
Number of 4 input LUTs	:	1
Number of IOs	:	5
Number of bonded IOBs	:	5
Macros	:	1 Register, 1 Flip-Flops
Delay	:	Before clock: 2.495ns, after clock: 4.063ns

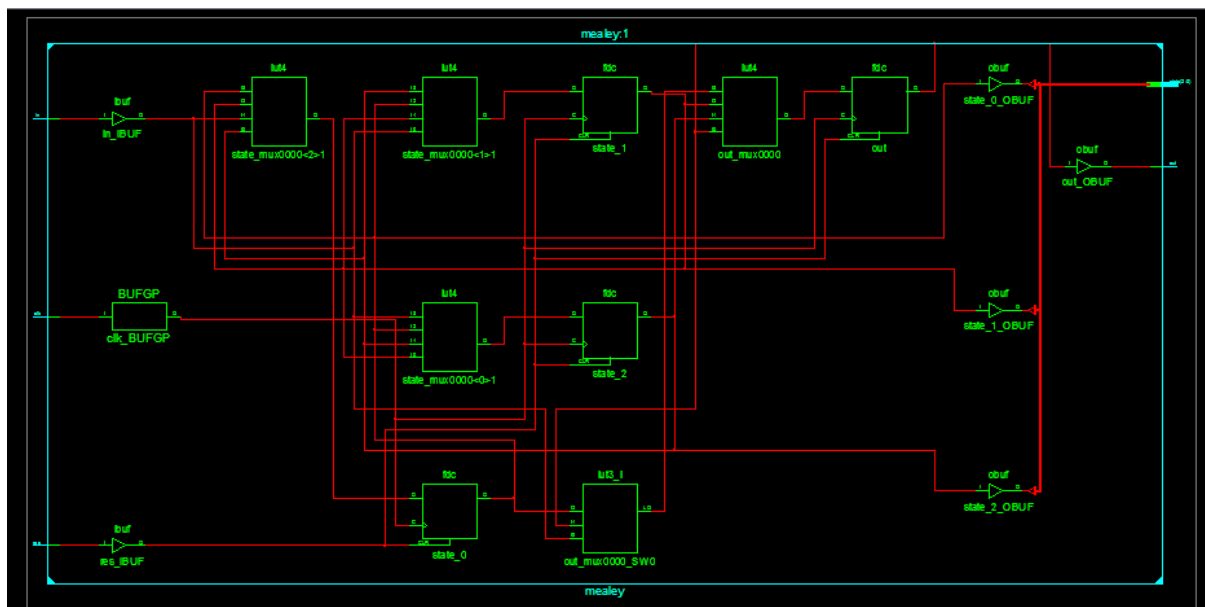

**Design statistics**

Number of Slices	:	3
Number of 4 input LUTs	:	5
Number of IOs	:	7
Number of bonded IOBs	:	7
Macros	:	4 Register, 4 Flip-Flops
Delay	:	Before clock: 2.677ns, after clock: 3.352ns